

ECE 317
Summer 2005
Lab Assignment #4

Passive Filter Design

- 1) Design a first order low-pass filter with a cutoff frequency of 2.5 kHz. Assume that only a 0.22 μF capacitor is available.
 - A) Show how you designed the filter. List all component values and include the circuit schematic.
 - B) Use PSpice to verify your design by plotting the magnitude response (in dB) and phase response (in degrees) of the filter.
 - C) What is the frequency where the magnitude response is -10 dB?
 - D) What is the frequency where the phase response is -45° ?

- 2) Design a second order high-pass filter to filter out the signal $x_1(t)$ and pass the signals $x_2(t)$ and $x_3(t)$ from the composite signal $x(t) = x_1(t) + x_2(t) + x_3(t)$, where $x_1(t) = 0.9 \cos(3,000\pi t - \pi/2)u(t)$, $x_2(t) = 1.1 \cos(18,000\pi t)u(t)$, and $x_3(t) = \cos(12,000\pi t + 2\pi/3)u(t)$. Assume that only a 0.47 μF capacitor is available.
 - A) Show how you designed the filter. List all component values and include the circuit schematic.
 - B) Explain your choices for the cutoff frequency (ω_c) and quality factor (Q).
 - C) Use PSpice to verify your design by plotting the magnitude response (in dB) of the filter.
 - D) What is the attenuation (in dB) of the filter at each of the three input frequencies?
 - E) Give an expression for the steady-state output of the filter, $y_{ss}(t)$. Provide numerical values for the amplitudes and phase shifts (in radians).

- 3) Design a filter to pass the frequency band $124 \text{ kHz} \leq f \leq 136 \text{ kHz}$ and filter out any other frequencies. Assume that only a 75 pF capacitor is available.
- A) Show how you designed the filter. Include the center frequency (f_0), quality factor (Q), all the component values, and the circuit schematic.
 - B) Use PSpice to verify your design by plotting the magnitude response (in dB) of the filter.
 - C) If the value of the capacitor, C, is changed by 20%, 10%, 5%, -5%, -10% and -20% from its nominal value (75 pF), find the corresponding percent changes in the center frequency (f_0) and quality factor (Q). Thus, plot the percent change in f_0 (y-axis) vs. the percent change in C (x-axis) and the percent change in Q (y-axis) vs. the percent change in C (x-axis). Do the filter's center frequency and quality factor have a high or a low sensitivity to variations in the value of the capacitor?