


ECE 317
Summer 2005
Review Questions for Exam #2

General topics you should know for Exam #2:

- a) Circuit analysis using the Laplace transform
 - i) Without initial conditions
 - ii) With initial conditions
- b) Frequency response
 - i) Magnitude response
 - ii) Phase response
 - iii) Steady-state response to sinusoidal inputs
- c) Filters
 - i) Standard filter types
 - ii) Passive filter design

Questions:

1) Consider the following circuit:

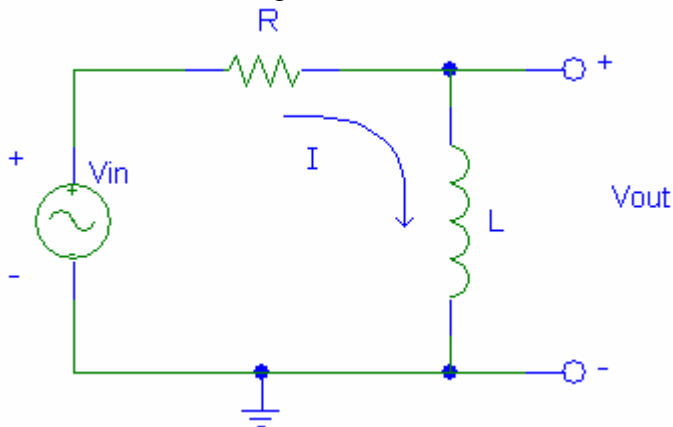

Assume that $V_{in}(t) = u(t)$, $R = 4 \Omega$, $L = 2 \text{ H}$, and the initial current flowing through the inductor is 1 A.


- A) Determine and sketch $i(t)$.
 - B) Determine and sketch $V_{out}(t)$.
- 2) Consider an LTI system with $H(s) = \frac{s}{s+3}$.
- A) Determine and sketch the step response.
 - B) Determine and sketch the steady-state response to an input $x(t) = 3 \cos(2t + \pi/2)u(t)$.

- 3) Consider a composite signal $x(t) = x_1(t) + x_2(t) + x_3(t)$, where $x_1(t) = 1.5 \cos(250\pi t)u(t)$, $x_2(t) = \cos(500\pi t + \pi/4)u(t)$, and $x_3(t) = 0.5 \cos(750\pi t)u(t)$. Assume that only a $4.20 \mu\text{F}$ capacitor is available.
- A) Design a passive second order filter to eliminate $x_2(t)$ and $x_3(t)$.
 - B) Design a passive second order filter to eliminate $x_1(t)$ and $x_3(t)$.

Solutions:

1)

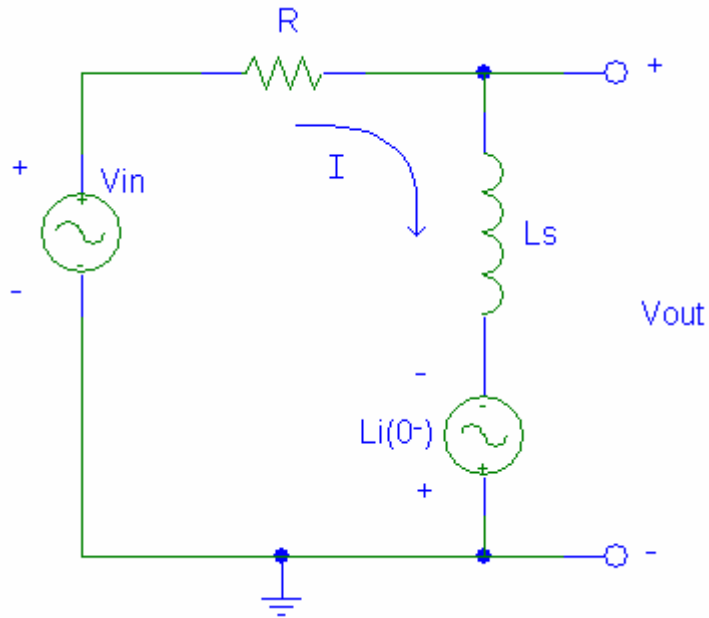A) $V_{in}(t) = u(t) \xrightarrow{LT} V_{in}(s) = 1/s$



From loop analysis:

$$0 = -V_{in}(s) + I(s)[R + Ls] - Li(0^-) \rightarrow I(s)[R + Ls] = V_{in}(s) + Li(0^-) \rightarrow$$


$$I(s) = \frac{V_{in}(s) + Li(0^-)}{R + Ls} = \frac{V_{in}(s)}{R + Ls} + \frac{Li(0^-)}{R + Ls} = \frac{(1/s)}{4 + 2s} + \frac{2(1)}{4 + 2s} = \frac{(1/s)}{4 + 2s} + \frac{2(1)}{4 + 2s}$$

$$= \frac{1}{2s(s+2)} + \frac{2}{2(s+2)} = \frac{0.5}{s(s+2)} + \frac{1}{s+2} = \frac{\alpha_1}{s} + \frac{\alpha_2}{s+2} + \frac{1}{s+2}$$

$$\alpha_1 = \left. \frac{0.5(s)}{s(s+2)} \right|_{s=0} = \left. \frac{0.5}{s+2} \right|_{s=0} = \frac{0.5}{0+2} = 0.25$$


$$\alpha_2 = \left. \frac{0.5(s+2)}{s(s+2)} \right|_{s=-2} = \left. \frac{0.5}{s} \right|_{s=-2} = \frac{0.5}{-2} = -0.25$$
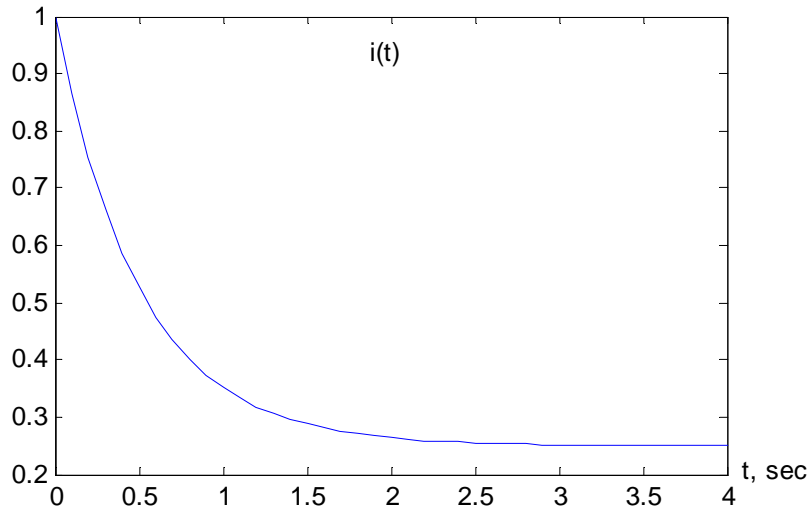
$$I(s) = \frac{0.25}{s} + \frac{-0.25}{s+2} + \frac{1}{s+2} = \frac{0.25}{s} + \frac{0.75}{s+2} \xrightarrow{LT^{-1}} i(t) = 0.25u(t) + 0.75e^{-2t}u(t)$$



$$\begin{aligned} \text{B) } V_{out}(t) = V_L(t) &= L \frac{di(t)}{dt} \xrightarrow{LT} LsI(s) - Li(0^-) = [2s]I(s) - 2 = (2s) \left[\frac{0.25}{s} + \frac{0.75}{s+2} \right] - 2 \\ &= \frac{0.5s}{s} + \frac{1.5s}{s+2} - 2 = 0.5 + \frac{1.5s}{s+2} - 2 = \frac{1.5s}{s+2} - 1.5 = \left[1.5 - \frac{3}{s+2} \right] - 1.5 = -\frac{3}{s+2} \end{aligned}$$

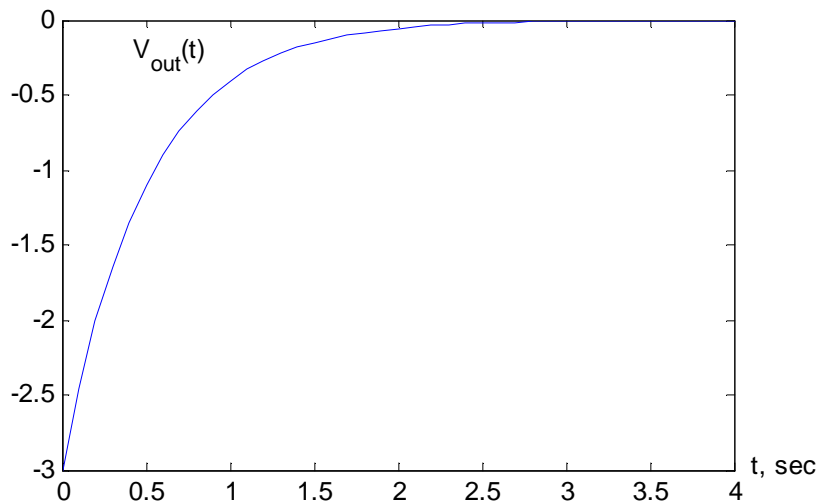
$$V_{out}(s) \xrightarrow{LT^{-1}} V_{out}(t) = -3e^{-2t}u(t)$$




2)

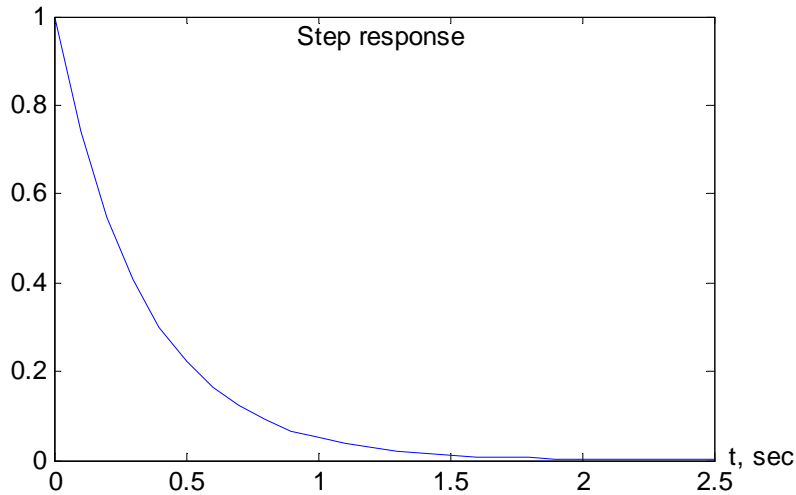A) $x(t) = u(t) \xrightarrow{LT} X(s) = 1/s$

$$Y(s) = X(s)H(s) = \frac{1}{s} \left(\frac{s}{s+3} \right) = \frac{1}{s+3} \xrightarrow{LT^{-1}} y(t) = e^{-3t}u(t)$$



B) $x(t) = 3\cos(2t + \pi/2)u(t)$

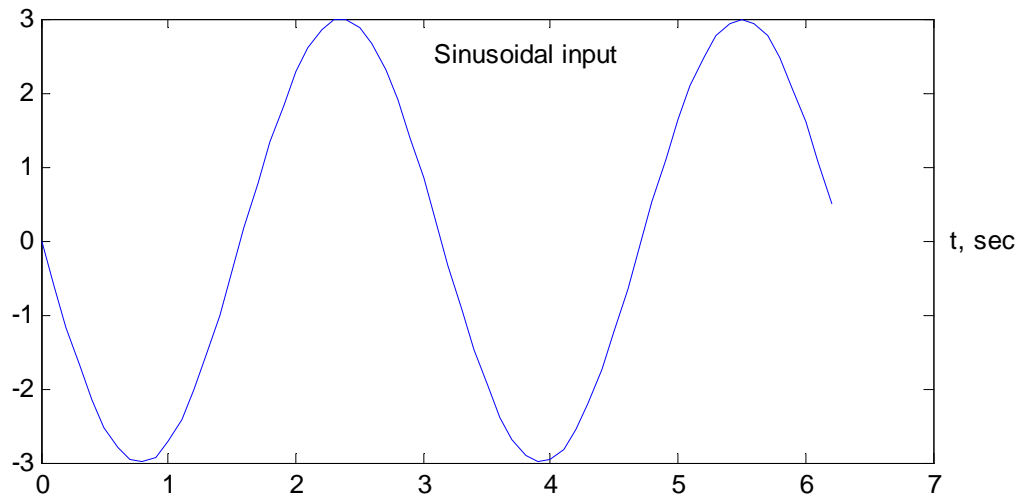

$$y_{ss}(t) = 3|H(j2)|\cos[2t + \pi/2 + \angle H(j2)]u(t)$$

$$H(j\omega) = H(s)|_{s=j\omega} = \frac{j\omega}{j\omega+3}$$


$$|H(j\omega)| = \frac{|j\omega|}{|j\omega+3|} = \frac{|\omega|}{\sqrt{3^2 + \omega^2}} = \frac{|\omega|}{\sqrt{9 + \omega^2}}$$

$$|H(j2)| = \frac{|2|}{\sqrt{9+2^2}} = \frac{2}{\sqrt{13}} = 0.5547$$

$$\angle H(j\omega) = \angle(j\omega) - \angle(j\omega + 3) = \pi/2 - \tan^{-1}(\omega/3) \quad \text{if } \omega > 0 \text{ rad/sec}$$

$$\angle H(j2) = \pi/2 - \tan^{-1}(2/3) = 0.9828 \text{ rad}$$
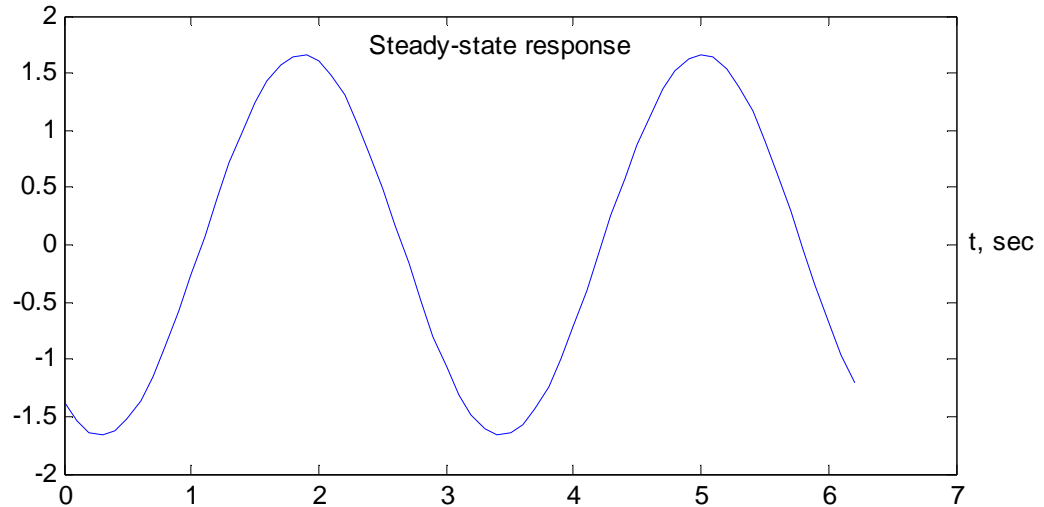
$$y_{ss}(t) = 3(0.5547)\cos[2t + \pi/2 + (0.9828)]u(t) = 1.6641\cos[2t + 2.5536]u(t)$$



- 3) Complete solution not available until lab assignment #4 is turned in.
- A) Assuming a second order low-pass filter with $\omega_c = 375\pi$ rad/sec, $R = 285.8147 \Omega$ and $L = 0.1715$ H.
 - B) Assuming a second order band-pass filter with $\omega_0 = 500\pi$ rad/sec and $BW = 250\pi$ rad/sec, $R = 75.7881 \Omega$ and $L = 0.0965$ H.