

**ECE 317**  
**Summer 2005**  
**Review Questions for Exam #3**

General topics you should know for Exam #3:

- a) Passive filter design
  - i) First order: low-pass, high-pass
  - ii) Second order: low-pass, high-pass, band-pass, notch
  - iii) Deriving the transfer function of a simple filter from its circuit
- b) Active filter design
  - i) First order: low-pass, high-pass, all-pass
  - ii) Second order: low-pass, high-pass (Sallen & Key)
  - iii) Deriving the transfer function of a simple filter from its circuit
- c) Fourier analysis
  - i) Magnitude response
  - ii) Phase response
  - i) Steady-state response to sinusoidal inputs
  - ii) Basic understanding of Fourier series expansion
  - iii) Parseval's theorem


Questions:

- 1) Design a first order filter with a constant magnitude response to produce a phase shift of  $\pi/2$  radians at a frequency of 30 kHz using only 400 pF capacitors.
  - A) Show how you designed the filter. Include the circuit schematic with all component values.
  - B) Use PSpice to verify your design by plotting the magnitude response (in linear scale) and phase response (in degrees) of the filter.
  
- 2) Design a third order active Butterworth high-pass filter with a cutoff frequency of 10 kHz using only 20 nF capacitors.

Hint: Follow the same procedure as you would for a low-pass filter, but use high-pass circuits. The required Q value is 1.


  - A) Show how you designed the filter. Include the circuit schematic with all component values.
  - B) Use PSpice to verify your design by plotting the magnitude response (in dB) and phase response (in degrees) of the filter.

3) Consider the following circuit:

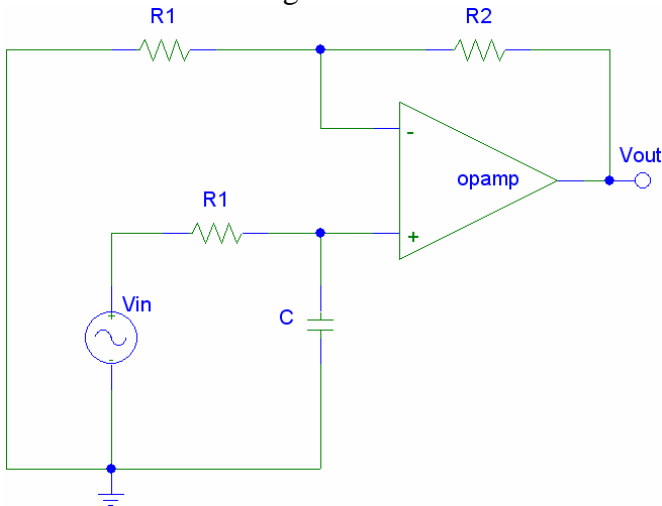

- Show that the transfer function of the circuit matches that of a standard first order low-pass filter.
- Express  $k_p$  and  $\omega_c$  in terms of the circuit components.
- Use this circuit to implement a low-pass filter with a cutoff frequency of 50 kHz and a DC gain of 1.5. Assume that the only available capacitor is 4.7 nF.

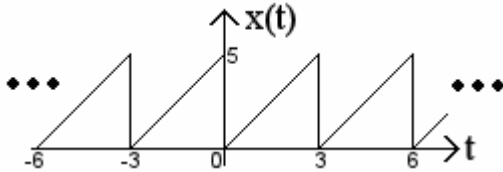4) Consider the following periodic signal:



If the Fourier series coefficients of  $x(t)$  are:

$$c_n = \begin{cases} c_0 & n = 0 \\ j \frac{5}{2\pi n} & n = \pm 1, \pm 2, \dots \end{cases}$$

- Calculate the value of  $c_0$ .
- What property of the signal does  $c_0$  represent?
- What is the normalized average power contained in the DC component and the first 2 harmonics (i.e. up to  $n = 2$ )?
- What percentage of the signal's total normalized average power is contained in the DC component and the first 2 harmonics?

Solutions:

1)


A) First order all-pass filter with  $k_p > 0$  (non-inverting) and  $f_0 = 30 \text{ kHz}$

$C = 400 \text{ pF}$


$k_p = 1$

$\omega_0 = 2\pi f_0 = 60,000\pi \text{ rad/sec}$

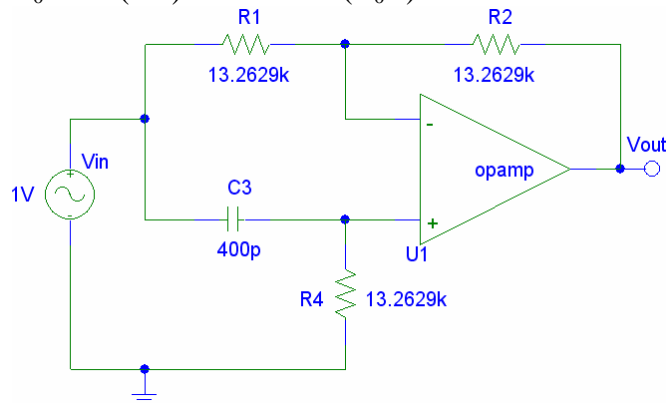
$\omega_0 = 1 / (RC) \rightarrow R = 1 / (\omega_0 C) = 13.263 \text{ k}\Omega$



B) Magnitude response (linear scale):

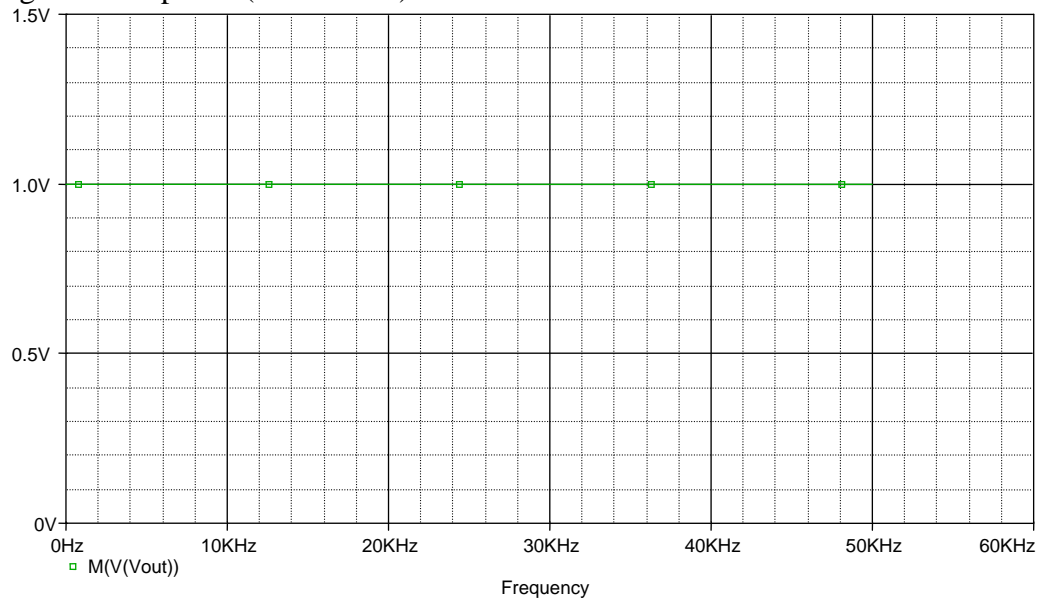

Phase response (degrees):

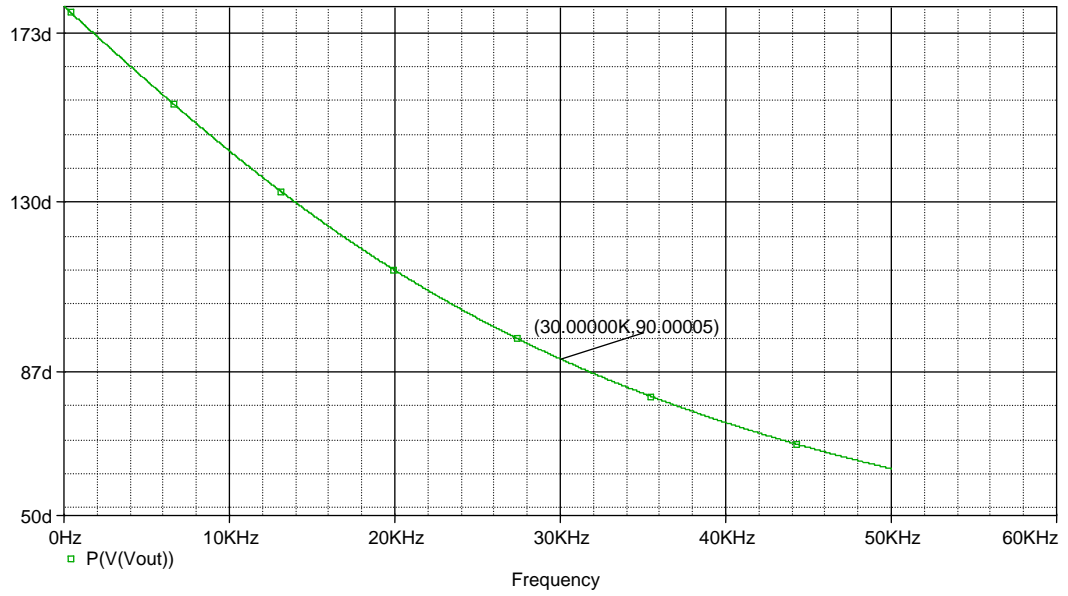

2)

A)  $C = 20 \text{ nF}$

$$\omega_c = 2\pi f_c = 20,000\pi \text{ rad/sec}$$

First order section:

$$\omega_c = 1 / (RC) \rightarrow R = 1 / (\omega_c C) = 795.77 \Omega$$

Second order section:


$$Q = 1$$

$$\omega_0 = \omega_c$$


$$\omega_c = 1 / (RC) \rightarrow R = 1 / (\omega_c C) = 795.77 \Omega$$

$$k_p = 3 - (1/Q) = 2$$


$$R_b = (k_p - 1)R = 795.77 \Omega$$

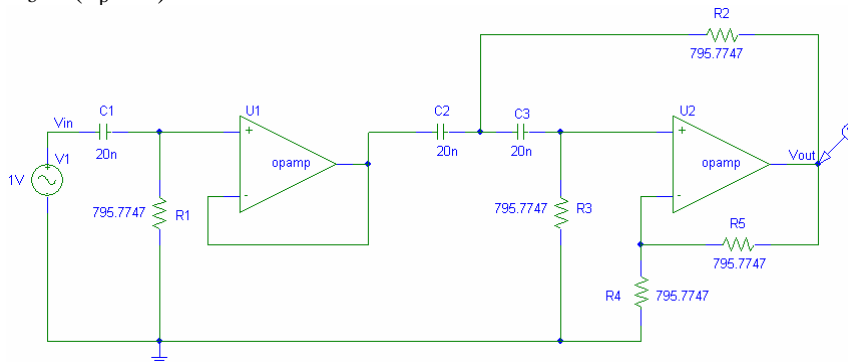

B) Magnitude response (in dB):

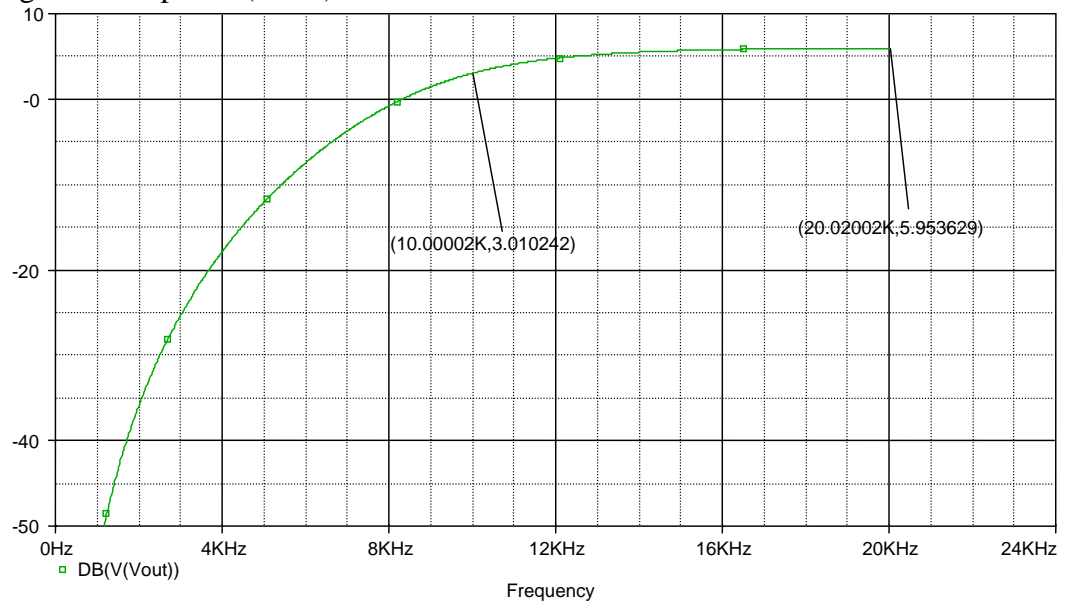

Phase response (degrees):

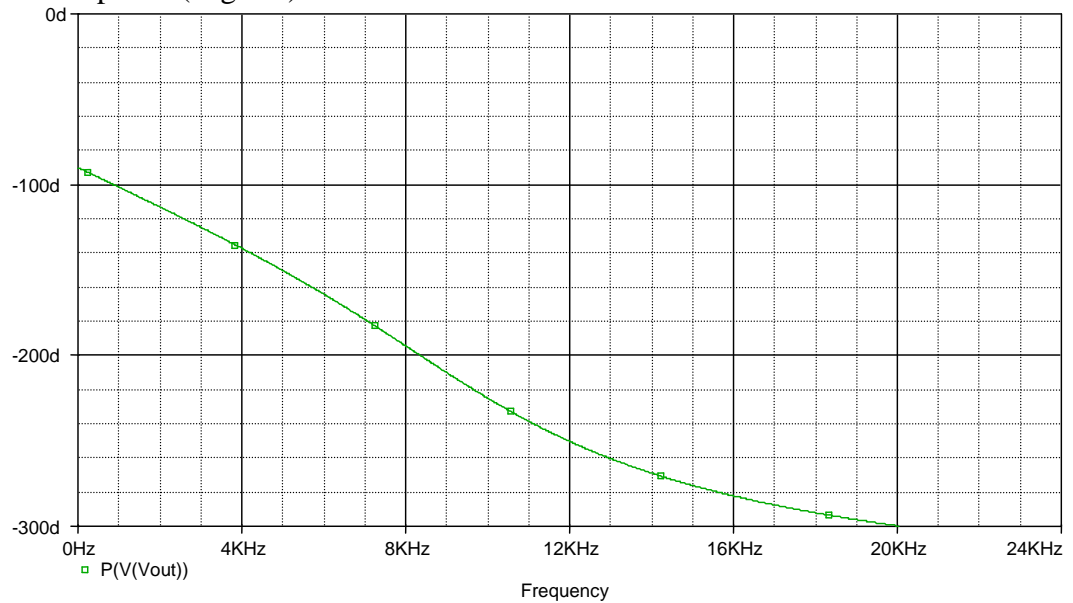

3)

$$A) \frac{V_{out}}{V_{in}} = H(s) = \frac{\left(\frac{R_2}{R_1} + 1\right) \left(\frac{1}{R_1 C}\right)}{s + \frac{1}{R_1 C}}$$

$$B) k_p = \frac{R_2}{R_1} + 1, \quad \omega_c = \frac{1}{R_1 C}$$


C)  $C = 4.7 \text{ nF}$

$$\omega_c = 2\pi f_c = 100,000\pi \text{ rad/sec}$$

$$k_p = 1.5$$

$$\omega_c = 1 / (R_1 C) \rightarrow R_1 = 1 / (\omega_c C) = 677.26 \Omega$$
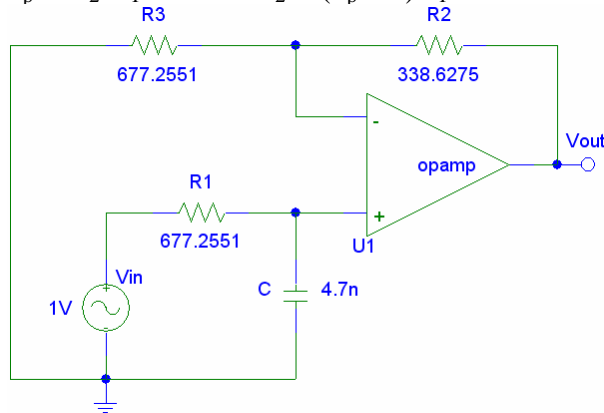
$$k_p = R_2 / R_1 + 1 \rightarrow R_2 = (k_p - 1)R_1 = 338.63 \Omega$$



4)

A)  $T_0 = 3 \text{ seconds}$

For  $0 \leq t \leq T_0$ , the slope =  $5/3$  and the y-intercept =  $0$ .

$$c_0 = \frac{1}{T_0} \int_{t_0}^{t_0+T_0} x(t) dt = \frac{1}{3} \int_0^3 \frac{5}{3} t dt = 2.5$$

B)  $c_0$  is the average value of the signal or the DC component of the Fourier series expansion.

$$C) P = \sum_{n=-\infty}^{\infty} |c_n|^2 = c_0^2 + 2 \sum_{n=1}^{\infty} |c_n|^2 = (2.5)^2 + 2 \sum_{n=1}^{\infty} \left| j \frac{5}{2\pi n} \right|^2$$

For DC and the first two harmonics:

$$P_2 = (2.5)^2 + 2 \sum_{n=1}^2 \left| j \frac{5}{2\pi n} \right|^2 = 6.25 + 2 \left( \left| j \frac{5}{2\pi(1)} \right|^2 + \left| j \frac{5}{2\pi(2)} \right|^2 \right)$$

$$P_2 = 7.8331 \text{ W}$$

$$D) P = \frac{1}{T_0} \int_{t_0}^{t_0+T_0} |x(t)|^2 dt = \frac{1}{3} \int_0^3 \left| \frac{5}{3} t \right|^2 dt = \frac{1}{3} \int_0^3 \frac{25}{9} t^2 dt = \frac{25}{27} \int_0^3 t^2 dt = \frac{25}{27} \frac{t^3}{3} \Big|_0^3 = \frac{25}{81} (3^3 - 0^3)$$

$$P = \frac{25}{81} (27) = \frac{25}{3} = 8.3333 \text{ W}$$

$$\frac{7.8331}{8.3333} (100\%) = 93.9977 \% \text{ of the total normalized average power}$$