

(a) Line parameters

$$Z_s = r_{a,c} + r_e + j \frac{\omega \mu}{2\pi} \ln \frac{D_e}{d} = 0.0001338 + j0.000911 \text{ ohms/m}$$

$$Z_{bc} = Z_{ab} = r_e + j \frac{\omega \mu}{2\pi} \ln \frac{D_e}{d_{ab}} = 0.00005929 + j0.000489 \text{ ohms/m}$$

$$Z_{ac} = r_e + j \frac{\omega \mu}{2\pi} \ln \frac{D_e}{d_{ac}} = 0.00005929 + j0.000436 \text{ ohms/m}$$

Computing TZT^{-1} , eliminating off diagonals, yields

$$Z_2 = Z_1 = 0.0000745 + j0.000439 \text{ ohms/m}$$

$$Z_0 = 0.000252 + j0.001853 \text{ ohms/m}$$

$$40 \text{ mile section of line} \Rightarrow Z_1 = Z_2 = 4.8 + j28.254 \text{ ohms}$$


$$Z_0 = 12.432 + j119.259 \text{ ohms}$$

Convert to pu

$$\text{Impedance Base} = Z_B = 115^2 / 100 = 132.25 \text{ ohm}$$

$$\Rightarrow Z_{1u} = Z_{2u} = 0.03629 + j0.2136$$

$$Z_{0u} = 0.094 + j0.90177$$

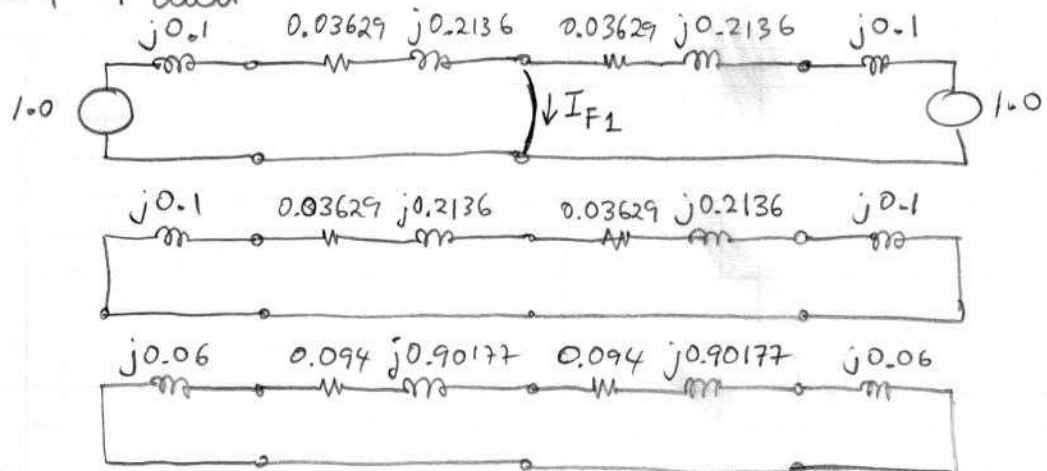3 ϕ Fault

$$\tilde{I}_{F1} = 2 \frac{1}{0.03629 + j0.3136} = 6.3352 e^{-j83.399^\circ}$$

$$I_{Base} = (100/3) / (115/\sqrt{3}) = 0.502 \text{ kA}$$

Fault Currents

$$\tilde{I}_{af} = 3.1805 \text{ kV } e^{-j83.399^\circ}$$

$$\tilde{I}_{bf} = 3.1805 \text{ kV } e^{-j203.399^\circ}$$

$$\tilde{I}_{cf} = 3.1805 \text{ kV } e^{-j323.399^\circ}$$

(Note $\tilde{I}_2 = \tilde{I}_0 = 0$)