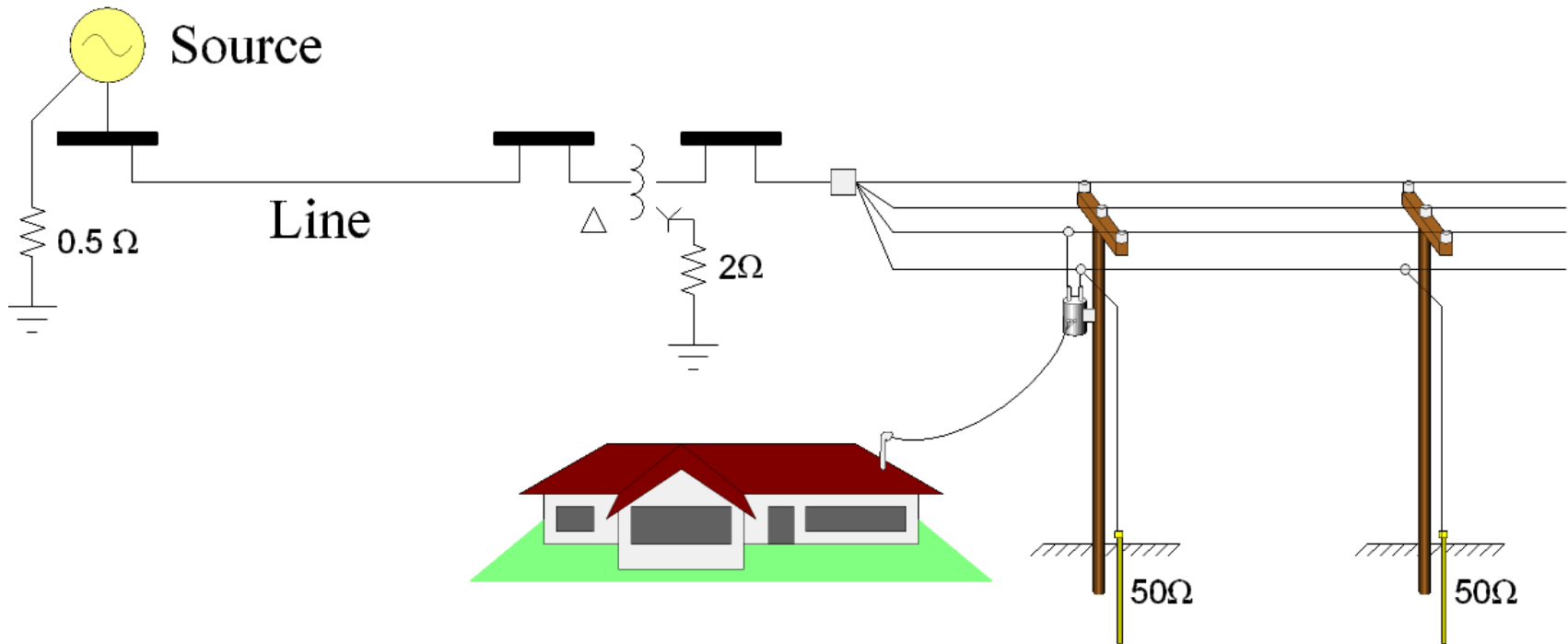


# Example: GPR Calculations



## Source:

$$Z_1 = Z_2 = j9.8 \text{ Ohms}$$

$$Z_0 = j6.6 \text{ Ohms}$$

$$Z_g = 0.5 \text{ Ohms}$$

## 115 kV Line:


$$Z_1 = Z_2 = 0.306 + j0.7362 \text{ Ohms/Mile}$$

$$Z_0 = 0.5285 + j2.99 \text{ Ohms/Mile}$$

115 kV Line Length: 23.5 miles

# Example GPR Calculations

## Distribution Line Model

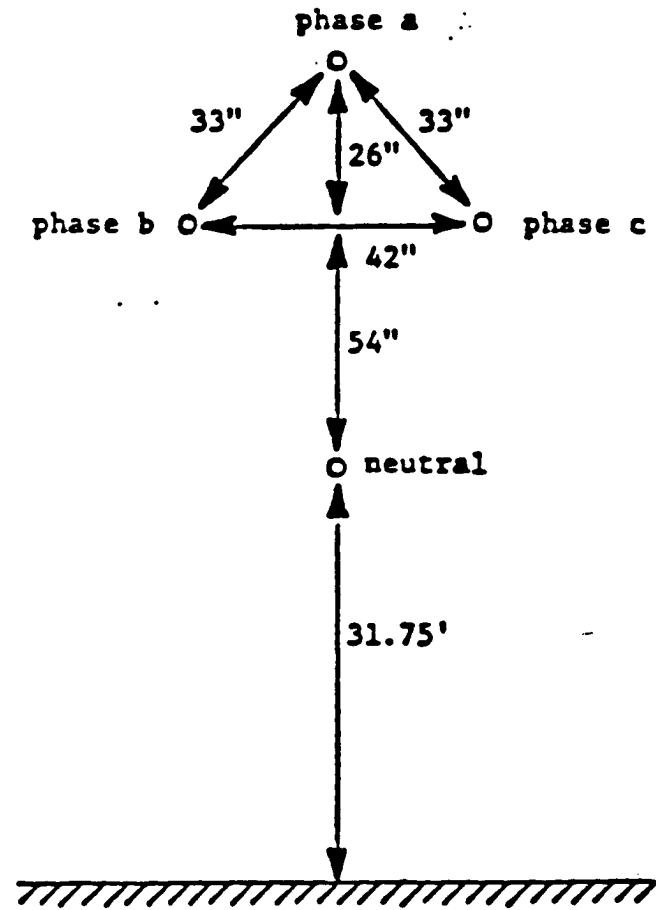


**Figure** Design of a 12 kV Distribution Line  
With a Neutral Conductor


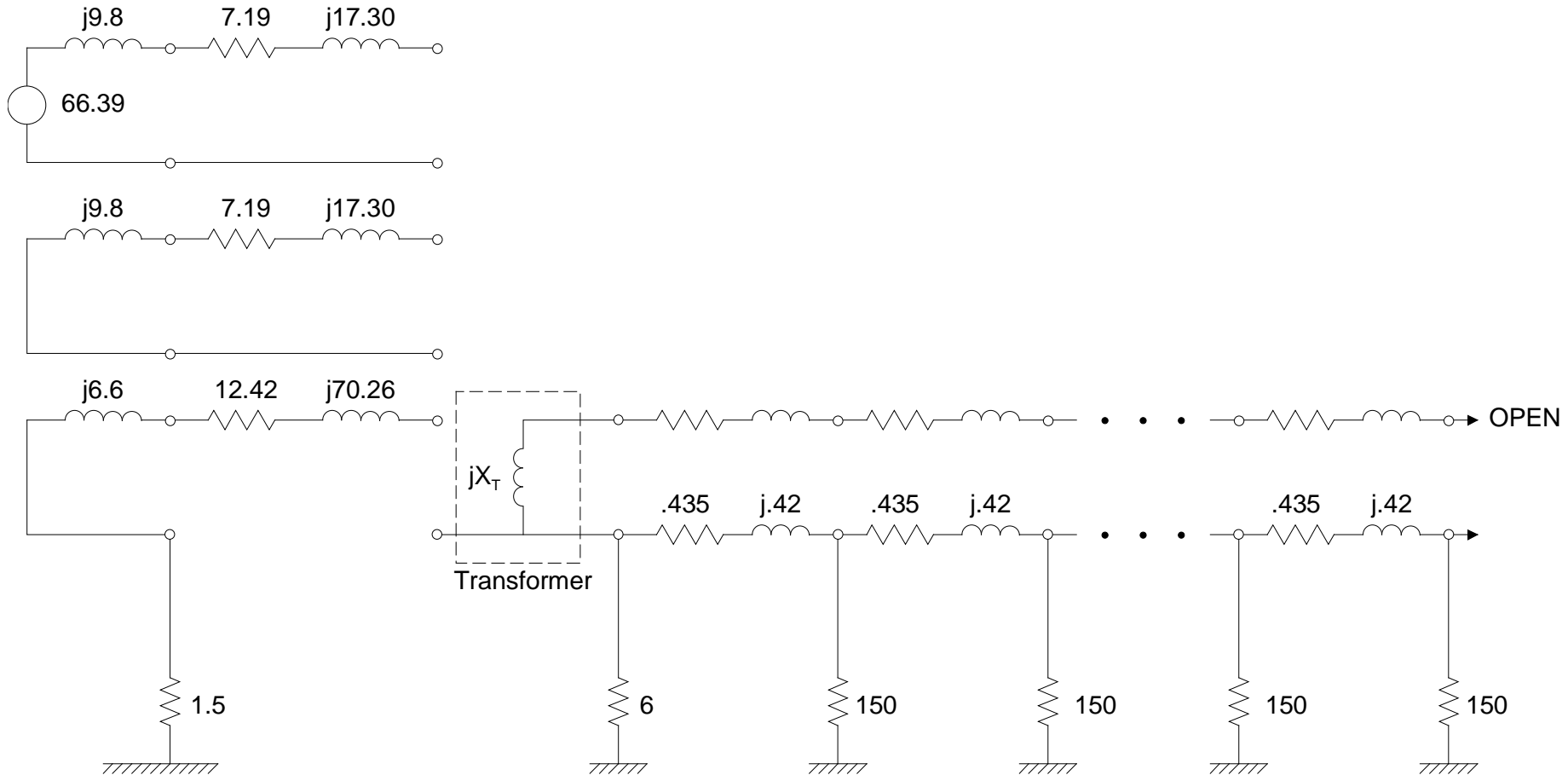
**Data:** Phase Conductor : 1/0 A  
Neutral Conductor : #2 A

# Example: GPR Calculations

## Sequence Networks



# Network Reductions

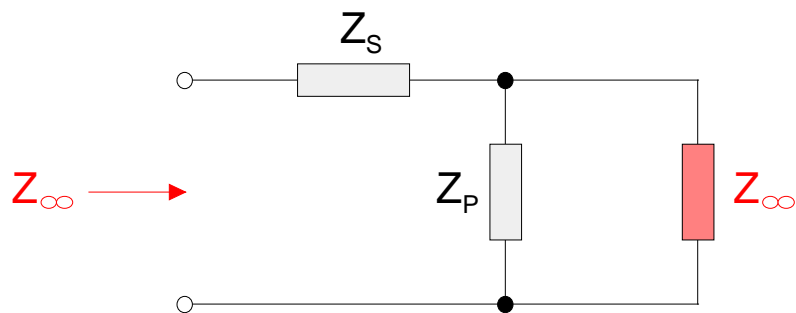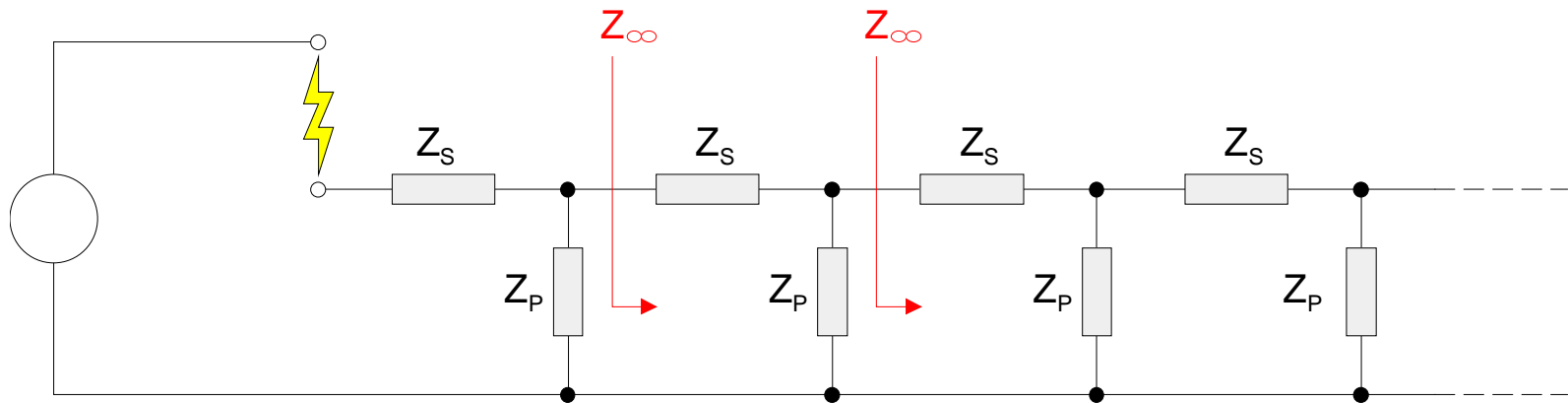

$$Z_{\infty} = \frac{Z_S}{2} + \sqrt{\left(\frac{Z_S}{2}\right)^2 + Z_S Z_P}$$

# Computation of GPR and Transfer Voltage

$$Z_S = 3 \left[ r_n + r_e + j(0.00466)(60) \log \left( \frac{D_e}{d_n} \right) \right] \ell_{span}$$

$$r_n = 1.65 \Omega / \text{mile}$$

$$r_e = 0.0954 \Omega / \text{mile}$$

$$D_e = 5380 \text{ feet}$$


$$d_n = 0.00504 \text{ feet}$$

$$\ell_{span} = 0.0833 \text{ miles} \quad (12 \text{ spans per mile})$$


$$Z_S = 0.435 + j0.42 \text{ ohms}$$

$$Z_\infty = \frac{Z_S}{2} + \sqrt{\left( \frac{Z_S}{2} \right)^2 + Z_S Z_T}$$
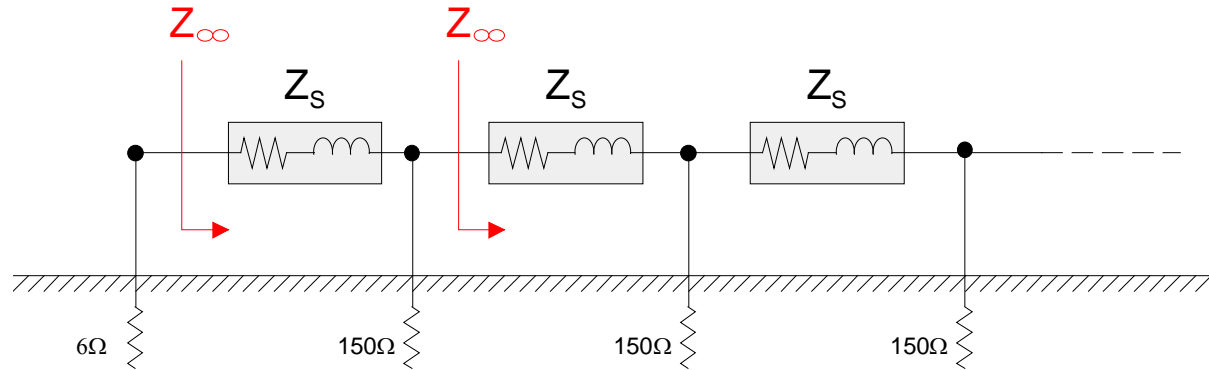
$$Z_\infty = 9.048 + j3.78 \text{ ohms}$$


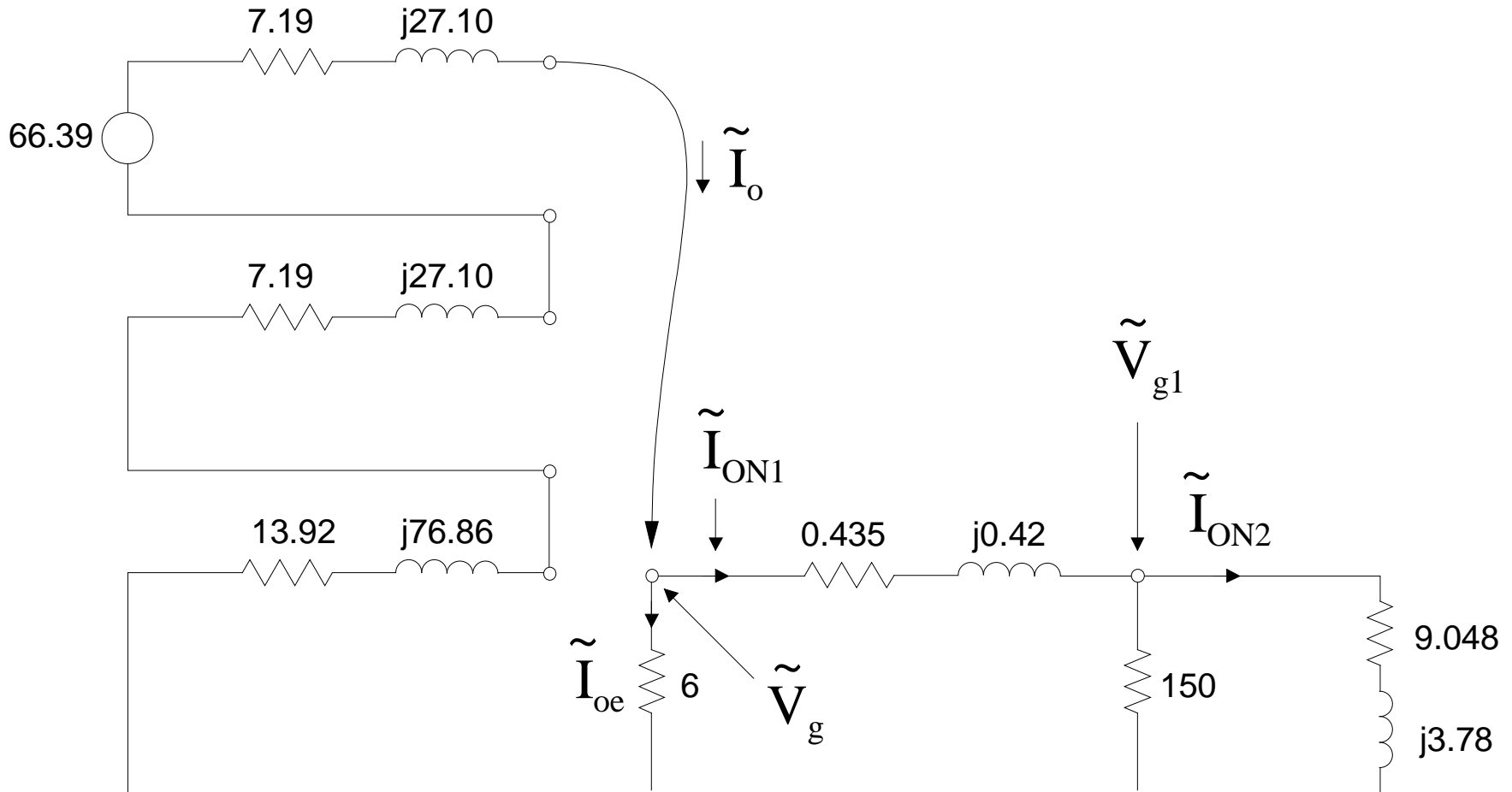
# Computation of GPR and Transfer Voltage



$$\tilde{I}_0 = 0.49e^{-j76.32^0} \text{ kA}$$

$$\tilde{V}_g = 1.858e^{-j67.75^0} \text{ kV}$$

$$\tilde{I}_{ON2} = 0.179e^{-91.79^0} \text{ kA}$$

$$\tilde{I}_{oe} = 0.31e^{-j67.75^0} \text{ kA}$$

$$\tilde{I}_{ON1} = 0.1894e^{-90.42^0} \text{ kA}$$

$$\tilde{V}_{g1} = 1.752e^{-j69.11^0} \text{ kV}$$