

CONTENTS

	PAGE
PREFACE	v
LIST OF SYMBOLS	xiii
CHAPTER 1	
PHYSICAL CONCEPTS	1
Excitation, ionization, and radiation	1
Ionization and excitation potentials	3
Structure of atoms	3
Types of ionization	4
Ionization by collision	5
Photo-ionization and ionization by cosmic rays	6
Space charge and space current	7
Deionization	7
Free electrons; electron affinity	9
Contact difference of potential	10
Emission of electrons and other ions from solids	11
Electron dynamics	13
Motion of electrons in electric fields	13
Electron transit time	16
Motion of electrons in magnetic fields	18
Problems	19
Bibliography	20
CHAPTER 2	
THERMIONIC EMISSION. THE HIGH-VACUUM DIODE	21
Physical theory of thermionic emission	21
Richardson's equation	23
Tungsten and thoriated tungsten emitters	25
Electron microscopes in the study of activation	27
Oxide-coated emitters	29
Cesiated tungsten emitters	31
Mechanical construction of cathodes	31
Effects of gas upon emission and space currents; getters	32
Limitation of anode current by space charge	34
Child's law	36
Deviations from Child's law observed in practical diodes	38
Plate dissipation	41
Tube classification	41

	Page
Structure of typical glass and metal tubes	45
Bibliography	46
CHAPTER 3	
GRID-CONTROLLED HIGH-VACUUM TUBES	48
Value of the grid	48
Theory of grid action in triodes	49
Functional equations for plate and grid currents	51
Time of transit of electrons	53
Static and dynamic characteristics	53
Tube factors	57
Relation of tube factors to characteristic curves	60
Sharp-cutoff and remote-cutoff grids; variable- μ tubes	62
The screen-grid tetrode	63
The space-charge tetrode	66
The suppressor pentode	67
The beam pentode	71
Duplex and multigridded tubes	73
Applied voltages in grid and plate circuits; load impedance	74
Form of alternating-plate-current wave	74
Static and dynamic operating points	75
Symbols for electrode voltages and currents	76
Voltage and current relations in grid and plate circuits	78
Harmonic generation	79
Series expansion for alternating plate current	80
Intermodulation	82
Relation of series coefficients to characteristic curves	85
Dynamic plate resistance	87
Problems	88
CHAPTER 4	
METHODS OF ANALYSIS OF VACUUM TUBES AND VACUUM-TUBE CIRCUITS	89
Equivalent electrode circuits	89
Tube capacitances and admittances	93
Static load line	96
Dynamic path of operation; dynamic load line	98
The plate diagram	99
Applications of the plate diagram	102
Graphical analysis of electrode currents	103
Percentage distortion and distortion factor	109
Graphical determination of power output	110
Problems	110
Supplementary bibliography	112
CHAPTER 5	
AMPLIFIER DEFINITIONS, CLASSIFICATIONS, AND CIRCUITS	114
Types of amplifier distortion	114
Voltage, current, and power amplifiers	117

CONTENTS

ix

	PAGE
Amplifier circuits	118
Frequency range of amplifiers	127
Class A, Class AB, Class B, and Class C amplifiers	127
The decibel and the volume unit	130

CHAPTER 6

ANALYSIS AND DESIGN OF AMPLIFIERS.	132
Single-tube amplifier with impedance load	132
Direct-coupled amplifier	135
Impedance-capacitance-coupled amplifier	136
Resistance-capacitance-coupled amplifier	137
Transformer-coupled audio-frequency amplifier	143
Comparison of resistance-coupled and transformer-coupled audio-frequency amplifiers.	147
Inductance-coupled audio-frequency amplifier	148
Choice of tubes for audio-frequency voltage amplifiers.	148
Control of amplification of audio-frequency amplifiers.	149
Tone control.	150
Tuned radio-frequency amplifiers.	150
Use of by-pass condensers to prevent oscillation	151
Limitation of amplification.	153
Measurement of voltage amplification.	154
Determination of frequency response of amplifiers.	155
Current amplifiers	155
Trigger circuits.	156
Methods of analysis of power amplifiers	157
Power relations in vacuum-tube plate circuits	158
Plate dissipation, power output, and plate-circuit efficiency.	159
Optimum power output	161
Class A1 triode power amplifiers	162
Class A1 pentode power amplifiers	163
Graphical determination of the performance of Class A1 power amplifiers	166
Measurement of power output	167
Experimental determination of optimum power output and optimum load	167
Push-pull power amplifiers.	169
Class AB power amplifiers.	170
Turn ratio of output transformer.	171
Inverse-feedback amplifiers.	171
Problems	173
Supplementary bibliography	176

CHAPTER 7

MODULATION AND DETECTION	179
Need for modulation; definition of modulation	179
Basic theory of amplitude modulation.	180

	PAGE
Amplitude modulation by characteristic curvature	183
Amplitude modulation by complete rectification	186
Linear-plate and linear-grid modulation	189
Detection of amplitude-modulated waves	190
Detection by curvature of current-voltage characteristics	190
Detection by complete rectification; linear diode detection	193
Linear plate detection and linear grid detection	197
Radio communication by means of amplitude-modulated waves	198
Basic theory of frequency modulation	199
Phase modulation	203
Frequency-modulation circuits	204
Detection of frequency-modulated voltages	206
Advantages of frequency modulation in radio communication	210
Problems	211
Supplementary bibliography	212
 CHAPTER 8 	
VACUUM-TUBE OSCILLATORS	214
Types of oscillators	214
Negative resistance oscillators	215
Feed-back oscillators	218
Limitation of amplitude of oscillation	222
Frequency stability; crystal and magnetostriction oscillators	224
Beat-frequency oscillators	226
Resistance-tuned oscillators	227
Relaxation oscillators	229
Use of relaxation oscillators in frequency transformation	231
Problems	232
 CHAPTER 9 	
GLOW- AND ARC-DISCHARGE TUBES	233
Current-voltage characteristics of glows	233
Physical aspects of the glow discharge	237
Potential distribution in the glow discharge	239
<i>Normal</i> and <i>abnormal</i> glow	240
Applications of glow tubes	241
The glow tube as a voltage stabilizer	242
The glow-tube relaxation oscillator	242
Grid control of glow discharges	245
Grid-glow-tube circuits	248
Starter-anode glow tubes	250
Arc discharges	250
Arc-discharge tubes with separately heated cathodes	252
Tungar rectifier	253
Cathode structure of low-pressure hot-cathode arc tubes	254
Choice of gas or vapor for arc tubes	256
Grid control of arcs; the thyatron	257
Grid current of thyatrons previous to firing	259

CONTENTS

xi

	PAGE
Control of arc-tube firing by means of an external grid	260
Magnetic control of thyratrons	260
Deionization in thyratrons	260
Voltage and current ratings of thyratrons and phanatrons	262
Electrode structure and characteristics of thyratrons	263
Comparison of thyratrons and high-vacuum tubes	268
Precautions required in the use of arc tubes	269
Applications of hot-cathode arc-discharge tubes	270
The hot-cathode arc diode as a rectifier	271
The thyatron as a d-c control device	271
The parallel arc-extinction circuit	272
Thyatron inverters	273
The thyatron as a saw-tooth-wave generator	277
A-c operation of thyratrons; phase control	280
Phase-control circuits	284
Use of saturable reactor in phase-control circuits	289
Applications of phase-control circuits	290
Thyatron welding control	290
Mercury-pool arc-discharge tubes	292
Arc initiation by means of an igniter	294
Ignitron structure	295
Comparison of thyratrons and ignitrons	297
Ignitron circuits	298
Applications of ignitrons	300
The strobotron	301
Stroboscopes	302
Problems	304

CHAPTER 10

LIGHT-SENSITIVE TUBES AND CELLS	305
Types of photoelectric phenomena	305
Historical survey	305
Laws of photoelectric emission	306
Current-wave-length characteristics	307
Light units	309
Current-voltage characteristics of the vacuum phototube	309
Phototube sensitivity	311
Theory of the gas phototube; gas phototube characteristics	312
Phototube circuits	315
Sensitivity of phototube and direct-coupled amplifier	320
The anode diagram and its use	321
Design of phototube circuits	323
Photoconductive cells	324
Photovoltaic cells	327
Comparison of phototubes, photoconductive cells, and photovoltaic cells	332
Problems	332
Supplementary bibliography	334

	PAGE
CHAPTER 11	
RECTIFIERS AND FILTERS	336
Definitions	336
Wave form of rectified current	338
Choice of rectifier tubes and circuit	339
Characteristics of rectifier circuits	341
Smoothing filters	344
Analysis of condenser filter	345
Voltage doublers	346
Design of choke-condenser (L -section) filters	347
Voltage stabilizers	349
Illustrative problem	351
Problems	353
Supplementary bibliography	353
CHAPTER 12	
ELECTRON-TUBE INSTRUMENTS	354
Advantages of vacuum-tube voltmeters	354
Plate-detection voltmeters	354
Diode voltmeters	358
Slide-back voltmeters	362
Cathode-ray tubes and oscillographs	364
Electron-ray tubes	369
Problem	370
APPENDIX	371
Chart for the determination of reactance	371
Chart for the determination of decibel gain	372
Plate characteristics of typical amplifier tubes	373
Operation characteristics of typical rectifier tubes	378
Operating data for typical amplifier tubes	379
AUTHOR INDEX	381
SUBJECT INDEX	387
ANSWERS TO PROBLEMS	395